

# Analog IC Design – Cadence Tools


## Lab 01

### LPF Simulation and MOSFET Characteristics

## PART 1: Low Pass Filter Simulation (LPF)

### 1. Transient Analysis

Design a first order low pass filter.

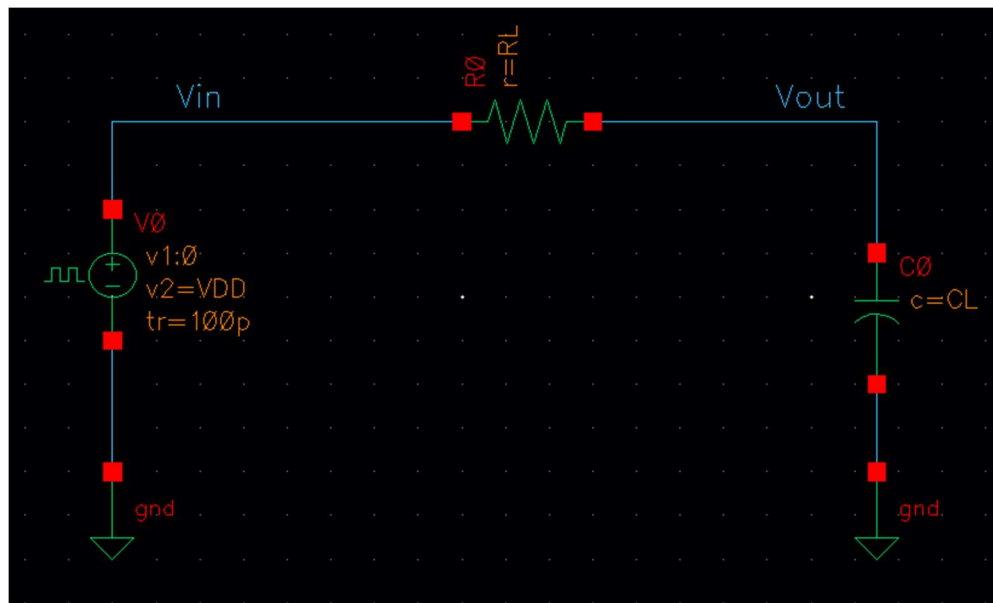

$R = 1k\Omega$  2 ns time constant

$$2n/1k = 2p \gg CL$$

Apply a square wave input with  $T_{high} = \text{Pulse Width} = 10ns$ ,  $T_{clk} = \text{Period} = 20ns$ , and  $T_{rise} = T_{fall} = 100ps$

PAC phase	
Voltage 1	0 V
Voltage 2	VDD V
Period	Tclk s
Delay time	Tclk/4 s
Rise time	100p s
Fall time	100p s
Pulse width	Thigh s
Temperature coefficient 1	

☒ Global Variables
 

<input checked="" type="checkbox"/> CL	2p
<input checked="" type="checkbox"/> RL	1k
<input checked="" type="checkbox"/> Tclk	20n
<input checked="" type="checkbox"/> Thigh	10ns
<input checked="" type="checkbox"/> VDD	1


Click to add variable

Report transient analysis results for two periods.


 
### Output Raining

ion started at: 9:02:14 PM, Mon Jun 24, 2024, ended at: 9:02:14 PM, Mon Jun 24, 2024, completes with 0 errors, 4 warnings, and 0 notices.




Calculate rise and fall time (10% to 90%) using Cadence calculator expressions. Export the expressions to adexl.

Test	Output	Nominal	Spec	Weight	Pass/Fail
part_1:lpf_tp:1	Vout				
part_1:lpf_tp:1	Vin				
part_1:lpf_tp:1	V0/PLUS				
part_1:lpf_tp:1	Trise	4.392n			
part_1:lpf_tp:1	Tfall	4.392n			

Compare simulation with analytical results in a table.

	Rise Time	Fall Time
<b>Analytical (<math>2.2 \cdot \tau</math>)</b>	4.4n	4.4n
<b>Simulation</b>	4.392n	4.392n

 Do parametric sweep for  $R = 1: 1: 5k\Omega$  Report overlaid results. Comment on the results.



Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: RL=1k						
1	part_1:lpf_tp:1	/Vout				
1	part_1:lpf_tp:1	/Vin				
1	part_1:lpf_tp:1	/V0/PLUS				
1	part_1:lpf_tp:1	Trise	4.392n			
1	part_1:lpf_tp:1	Tfall	4.392n			
Parameters: RL=2k						
2	part_1:lpf_tp:1	/Vout				
2	part_1:lpf_tp:1	/Vin				
2	part_1:lpf_tp:1	/V0/PLUS				
2	part_1:lpf_tp:1	Trise	8.771n			
2	part_1:lpf_tp:1	Tfall	8.771n			
Parameters: RL=3k						
3	part_1:lpf_tp:1	/Vout				
3	part_1:lpf_tp:1	/Vin				
3	part_1:lpf_tp:1	/V0/PLUS				
3	part_1:lpf_tp:1	Trise	eval err			
3	part_1:lpf_tp:1	Tfall	eval err			
Parameters: RL=4k						
4	part_1:lpf_tp:1	/Vout				
4	part_1:lpf_tp:1	/Vin				
4	part_1:lpf_tp:1	/V0/PLUS				
4	part_1:lpf_tp:1	Trise	eval err			
4	part_1:lpf_tp:1	Tfall	eval err			
Parameters: RL=5k						
5	part_1:lpf_tp:1	/Vout				
5	part_1:lpf_tp:1	/Vin				
5	part_1:lpf_tp:1	/V0/PLUS				
5	part_1:lpf_tp:1	Trise	eval err			
5	part_1:lpf_tp:1	Tfall	eval err			

Comment on the results.


Increasing R results in Increasing  $\tau$  >> linearly proportional

with  $\tau$  increasing the cutoff frequency decrease

but both the rise time and fall times increase. In case of  $\{R = 3K\Omega - R = 4K\Omega - R = 5K\Omega\}$  rise and fall times are bigger than pulse width so it cannot be calculated
 
## 2. AC Analysis

$$A_v = V_{out} / v_{in} \quad v_{in} = 1v \quad V_{out} = 1v$$




Analysis  $F = 1 / \text{Time constant} = 1/2\pi = 500M H$

Sweep Range

☒ Start-Stop      Start       Stop

☐ Center-Span

Sweep Type

 


Calculate DC gain and 3dB bandwidth using Cadence calculator expressions. Export the expressions to adexl.

$$H(S) = V_{out}/V_{in} = 1/(1+SRC), \text{ DC gain } S = 0 \text{ then DC gain} = 1$$

$$3dB \text{ BW} = 1/2\pi RC \quad 500M/2\pi = 79.57M$$


Test	Output	Nominal	Spec	Weight	Pass/Fail
part_1:lpf_tp:1	LPF_out_magntude				
part_1:lpf_tp:1	out_phase				
part_1:lpf_tp:1	3db				
part_1:lpf_tp:1	B.W	79.51M			
part_1:lpf_tp:1	Gain	1			

 

Compare simulation with analytical results in a table.


	3db	Gain
<b>Analytical</b>	79.57M	1
<b>Simulation</b>	79.3884M	1

 Do parametric sweep for  $R = 1, 10, 100, 1000k\Omega$ . Report overlaid results. Comment on the results.



Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: RL=1k						
1	part_1:lpf_tp:1	LPF_out_magntude				
1	part_1:lpf_tp:1	out_phase				
1	part_1:lpf_tp:1	3db				
1	part_1:lpf_tp:1	B.W	79.51M			
1	part_1:lpf_tp:1	Gain	1			
Parameters: RL=10k						
2	part_1:lpf_tp:1	LPF_out_magntude				
2	part_1:lpf_tp:1	out_phase				
2	part_1:lpf_tp:1	3db				
2	part_1:lpf_tp:1	B.W	7.951M			
2	part_1:lpf_tp:1	Gain	1			
Parameters: RL=100k						
3	part_1:lpf_tp:1	LPF_out_magntude				
3	part_1:lpf_tp:1	out_phase				
3	part_1:lpf_tp:1	3db				
3	part_1:lpf_tp:1	B.W	795.1k			
3	part_1:lpf_tp:1	Gain	1			
Parameters: RL=1M						
4	part_1:lpf_tp:1	LPF_out_magntude				
4	part_1:lpf_tp:1	out_phase				
4	part_1:lpf_tp:1	3db				
4	part_1:lpf_tp:1	B.W	79.51k			
4	part_1:lpf_tp:1	Gain	1			



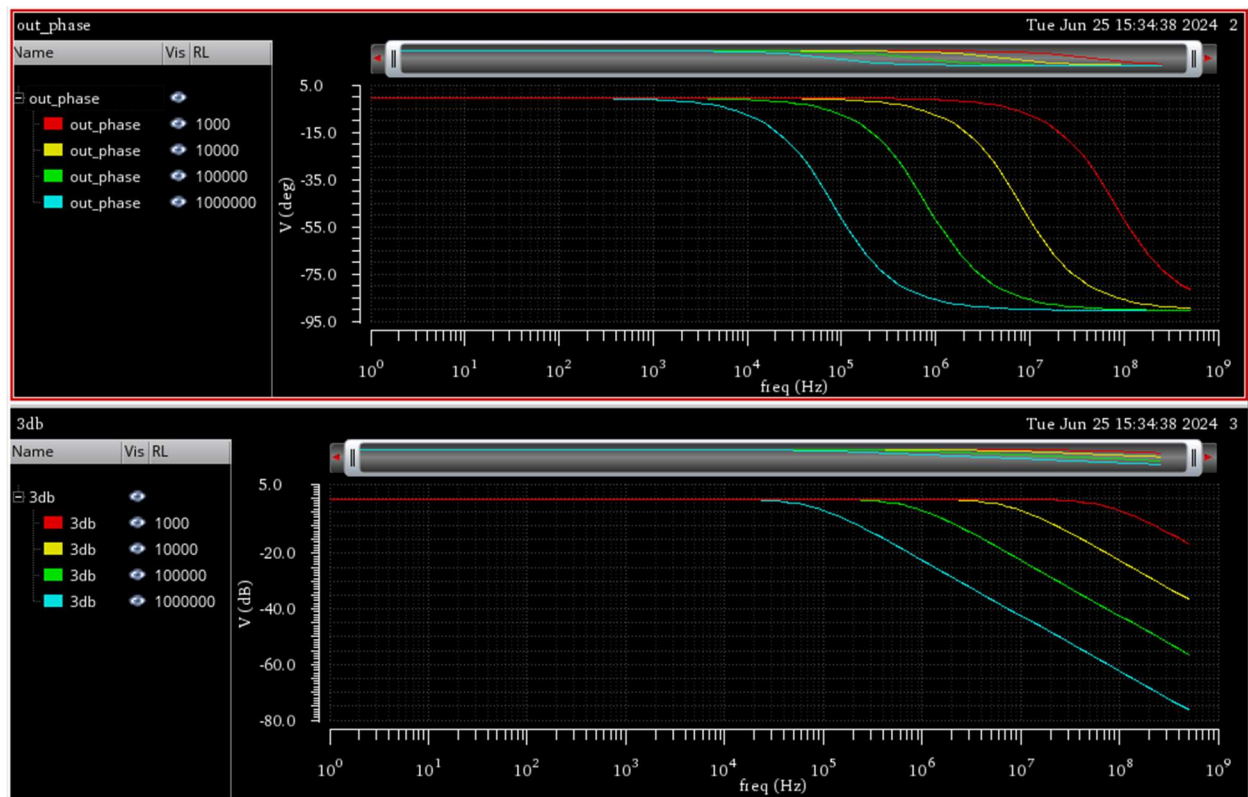


### COMMENT

DC gain does not depend on R or C, so it did not change.

while the bandwidth is inversely proportional to RC

When (RC) increases, (phase, B.W) decreases


## Part 2: MOSFET Characteristics

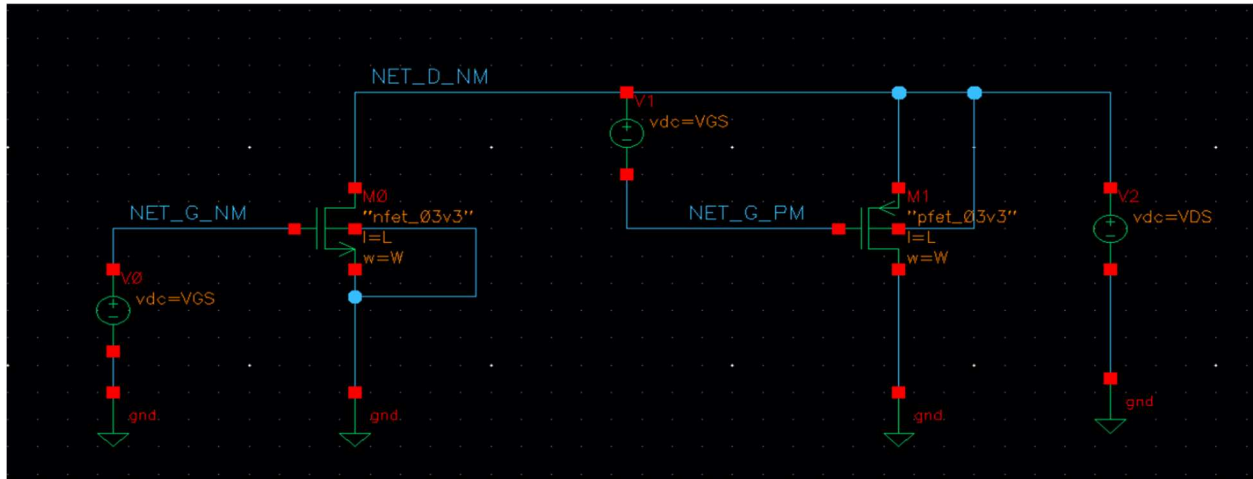

Plot  $ID - VGS$  characteristics for NMOS and PMOS devices. Set  $VDS = VDD$ , and  $VGS = 0: 10m: VDD$ . Use  $VDD = 1.2V$  for 130nm technology and  $VDD = 1.8V$  for 180nm technology. Plot the results overlaid for the following.


(Use  $VDD = 3V$ ) IN CANVAS use  $W/L = 3u/300n$  for the short channel device, and  $30u/3u$  for the long channel

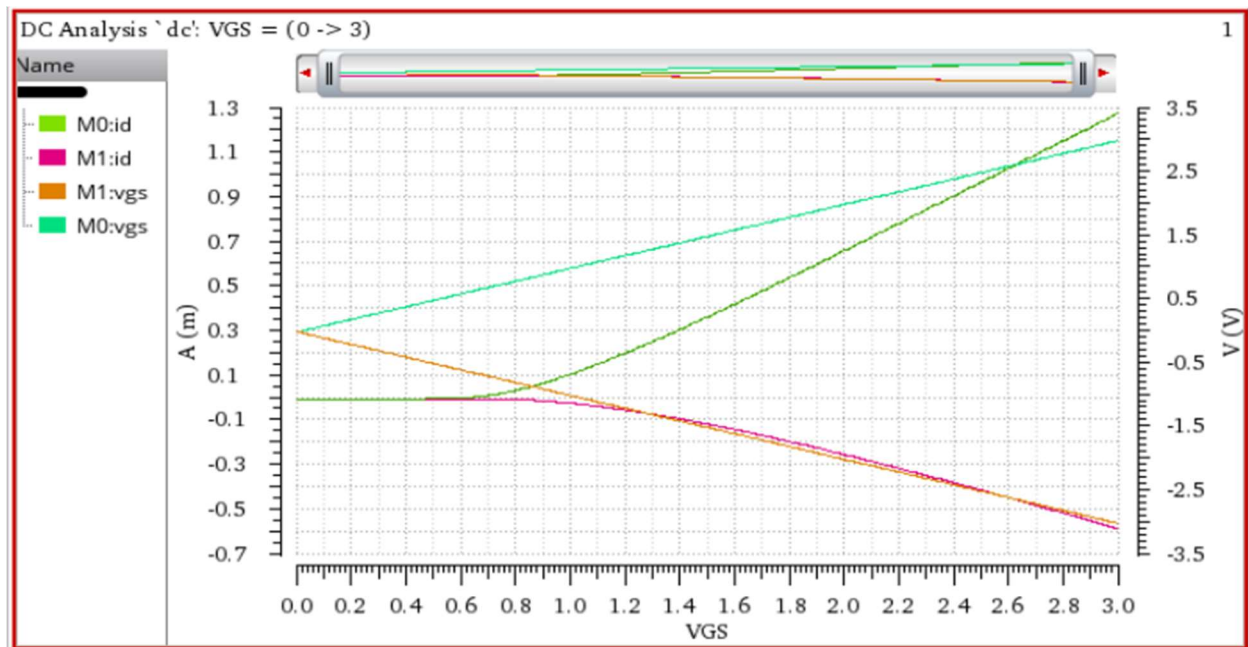Short channel device vdd=3v. (COMPARD {  $ID - VGS$  } TO NMOS & PMOS ).




 Long channel device vdd=3v (COMPARD {  $ID - VGS$  } TO NMOS & PMOS )






ID IN NMOS OF (SHORT & LONG )

 

## ID IN PMOS OF (SHORT & LONG )

 

### Comment on the differences between short channel and long channel results.

#### • Which one has higher current? Why?

For NMOS, a high-channel device provides a better display compared to a low-channel device. The reason for this is that the device suffers from a lack of weight due to its effect on speed saturation, which leads to a smaller output than usual, because it does not saturate before it reaches the starting point.

In case of PMOS devices, the current in the short-channel device is higher than the current in the long-channel device. This is due to the effect of voltage-induced barrier lowering (DIBL).

#### • Is the relation linear or quadratic? Why?

For short-channel devices, the relationship is linear, because the amplification factor ( $g_m$ ) reaches a saturated value and does not increase with increasing  $V_{gs}$ .

As for long-channel devices, the relationship is quadratic, as the amplification factor ( $g_m$ ) increases with increasing  $V_{gs}$ .

### Comment on the differences between NMOS and PMOS.

#### • Which one has higher current? Why?

NMOS device has the highest comparison with PMOS device. The reason for this is that the alternating current in an NMOS device consists of electrons, while the alternating current in a PMOS device consists of holes. Therefore, the electrons move faster than the holes.

#### • What is the ratio between NMOS and PMOS currents at $V_{GS} = V_{DD}$ ?

The ratio of the currents between the NMOS and PMOS devices at

$V_{GS} = V_{DD}$  un/up

. This is because both devices have the same bias and size, and differ only in the movement of the carriers


• **Which one is more affected by short channel effects?**

The NMOS device is more affected by short channel effects. This can be clearly seen from the graph of  $i_d$  vs  $v_{gs}$


## 2. $g_m$ vs $V_{GS}$

1) Plot  $g_m$  vs  $V_{GS}$  for NMOS device. Set  $V_{DS} = V_{DD}$ , and  $V_{GS} = 0: 10m: V_{DD}$ . Plot the results overlaid for the following:

Short channel device vdd=3v

 

Long channel device vdd=3v

 

## **2) Comment on the differences between short channel and long channel results.**

### **• Does $g_m$ increase linearly? Why?**

In case of a long channel device, increases.

$g_m$  is approximately linear because the device reaches the interruption saturation point before it reaches the speed saturation point and thus a relationship is formed.

ID-VGS quadratic, resulting in a linear relationship between

$g_m$ -VGS but in case of short channel device,

$g$  does not increase linearly.


### **• Does $g_m$ saturate? Why?**

In the case of a short channel device, it is saturated  $g_m$  at a certain value because the device reaches the speed saturation point before it reaches the interruption saturation point, thus a linear ID-VGS relationship is formed and  $g_m$  is saturated. But in the case of long channel device, The  $g_m$  does not saturate, but increases linearly

## **3. ID vs VDS**
 
### **• Q: Plot ID-VDS characteristics for NMOS device**





## 2) Comment on the differences between short channel and long channel results.

### • Which one has higher current? Why?

Long channel devices produce higher currents compared to short channel devices due to short channel effects, particularly velocity saturation.

### • Which one has higher slope in the saturation region? Why?

Short Channel devices have higher slope in saturation region as the slope of  $I_D$ ,  $V_{DS}$  is  $1/r_o$  and  $r_o$  Proportionate with  $L$ , so short channel devices have lower  $r_o$  which results in bigger slope